

1.

	1S complement	2S complement
10011100	01100011	01100100
10011101	01100010	01100011
1D101000	01010111	01011000
00000000	11111111	00000000
10000000	01111111	10000000

2.

a) $11010 - 10001$

$$\begin{array}{r} 1 \ 1 \ 1 \\ 11010 \\ + 01111 \\ \hline 101001 \end{array}$$

(discard end carry)

$\Rightarrow 11010 - 1001 = 01001$

b) $11110 - 1110 = 11110 - 01110$

$$\begin{array}{r} 1 \ 1 \ 1 \ 1 \\ 11110 \\ + 01110 \\ \hline 110000 \end{array}$$

(discard end carry)

$\Rightarrow 11110 - 1110 = 10000$

c) $1111110 - 1111110$

$$\begin{array}{r} 1 \ 1 \ 1 \ 1 \ 1 \ 1 \\ 1111110 \\ + 0000010 \\ \hline 10000000 \end{array}$$

(discard end carry)

$\Rightarrow 1111110 - 1111110 = 0000000$

$$d) 101001 - 101 = 101001 - 000101$$

$$\begin{array}{r} 11111 \\ 101001 \\ + 111011 \\ \hline 1100100 \end{array}$$

(discard end carry)

$$\Rightarrow 101001 - 101 = 100100$$



3.

$$\mathcal{D}_A = (B\bar{C} + \bar{B}C)x + (BC + \bar{B}\bar{C})\bar{x}$$

$$\mathcal{D}_B = \emptyset$$

$$\mathcal{D}_C = B$$

a)	Current state			Input x	Next state		
	$A(t)$	$B(t)$	$C(t)$		$A(t+1)$	$B(t+1)$	$C(t+1)$
	0	0	0	0	1	0	0
	0	0	0	1	0	0	0
	0	0	1	0	0	0	0
	0	0	1	1	1	0	0
	0	1	0	0	0	0	1
	0	1	0	1	1	0	1
	0	1	1	0	1	0	1
	0	1	1	1	0	0	1
	1	0	0	0	1	1	0
	1	0	0	1	0	1	0
	1	0	1	0	0	1	0
	1	0	1	1	1	1	0
	1	1	0	0	0	1	1
	1	1	0	1	1	1	1
	1	1	1	0	1	1	1
	1	1	1	1	0	1	1

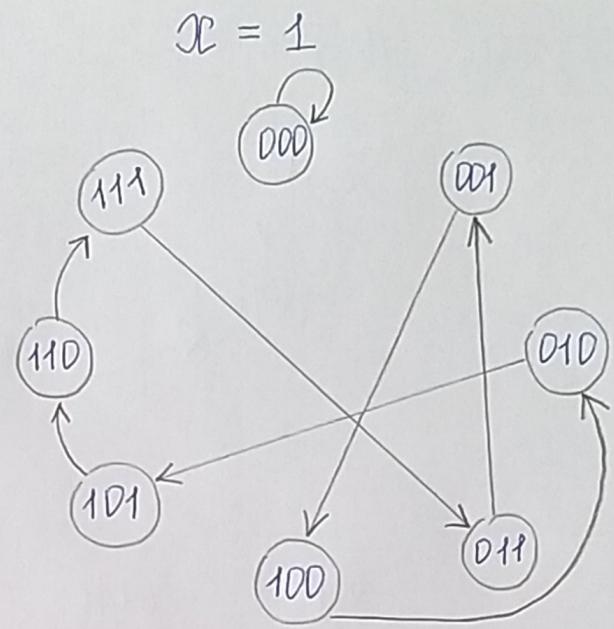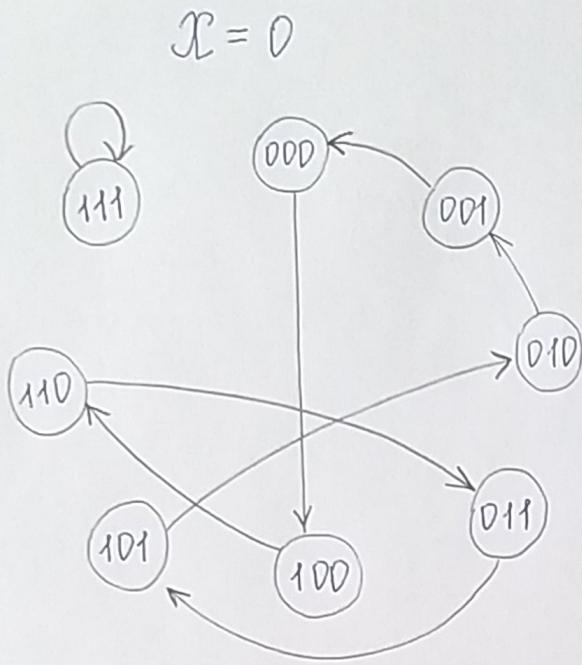


$$4. \quad \mathcal{D} = \mathcal{X} \oplus \mathcal{Y} \oplus \mathcal{S}$$


State table:

Current state $Q(t)$	Input		Next state $Q(t+1)$	Output S
	x	y		
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


State diagram:

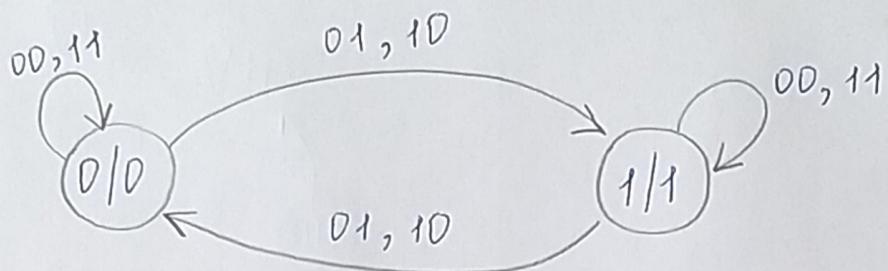

5.

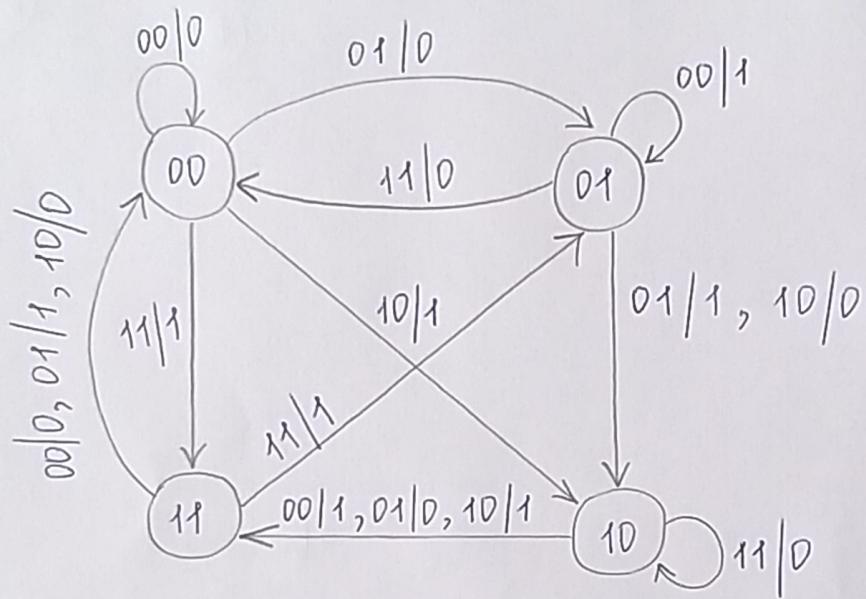

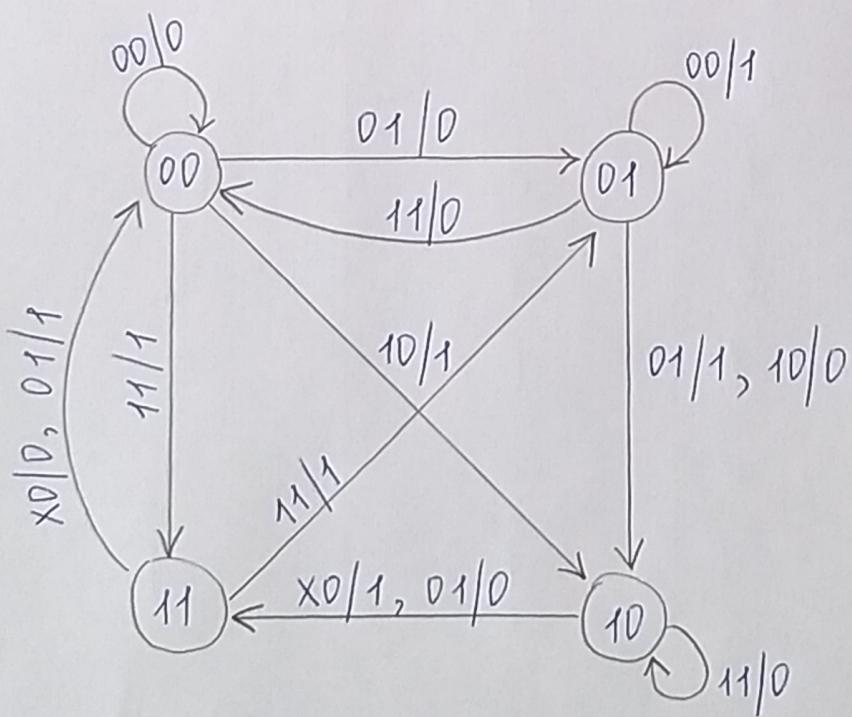State diagram can be simplified if $X = \text{unspecified}$:





6.

State table:

Current state		Input	Next state	
$A(t)$	$B(t)$	x	$A(t+1)$	$B(t+1)$
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1

$$A(t+1) = \mathcal{D}_A(A, B, x) = \sum_m (1, 4, 5, 6)$$
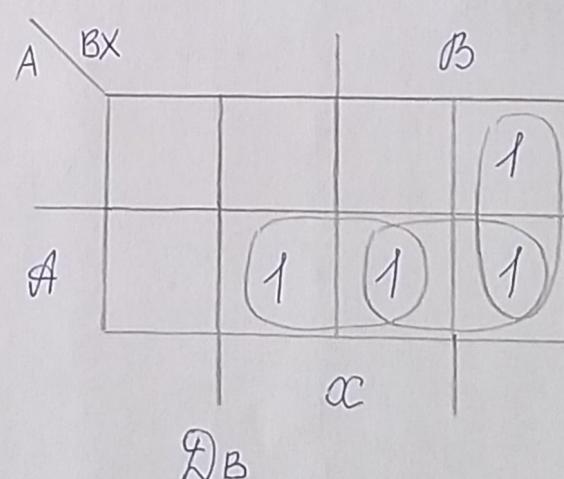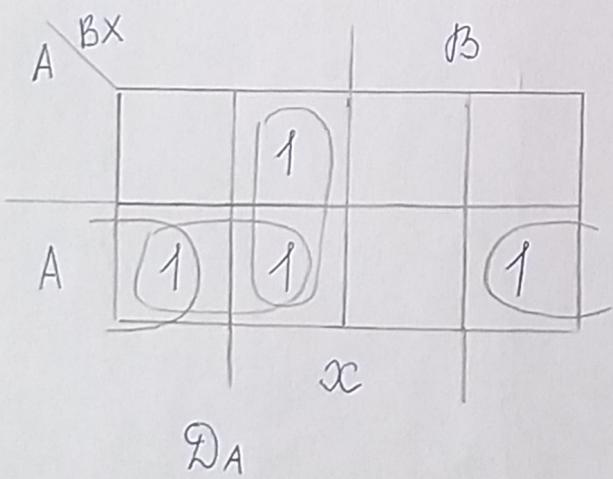
$$B(t+1) = \mathcal{D}_B(A, B, x) = \sum_m (2, 5, 6, 7)$$




Flip-flop input equations:

$$\mathcal{D}_A = A\bar{x} + \bar{B}x$$

$$\mathcal{D}_B = Ax + B\bar{x}$$

Logic diagram:

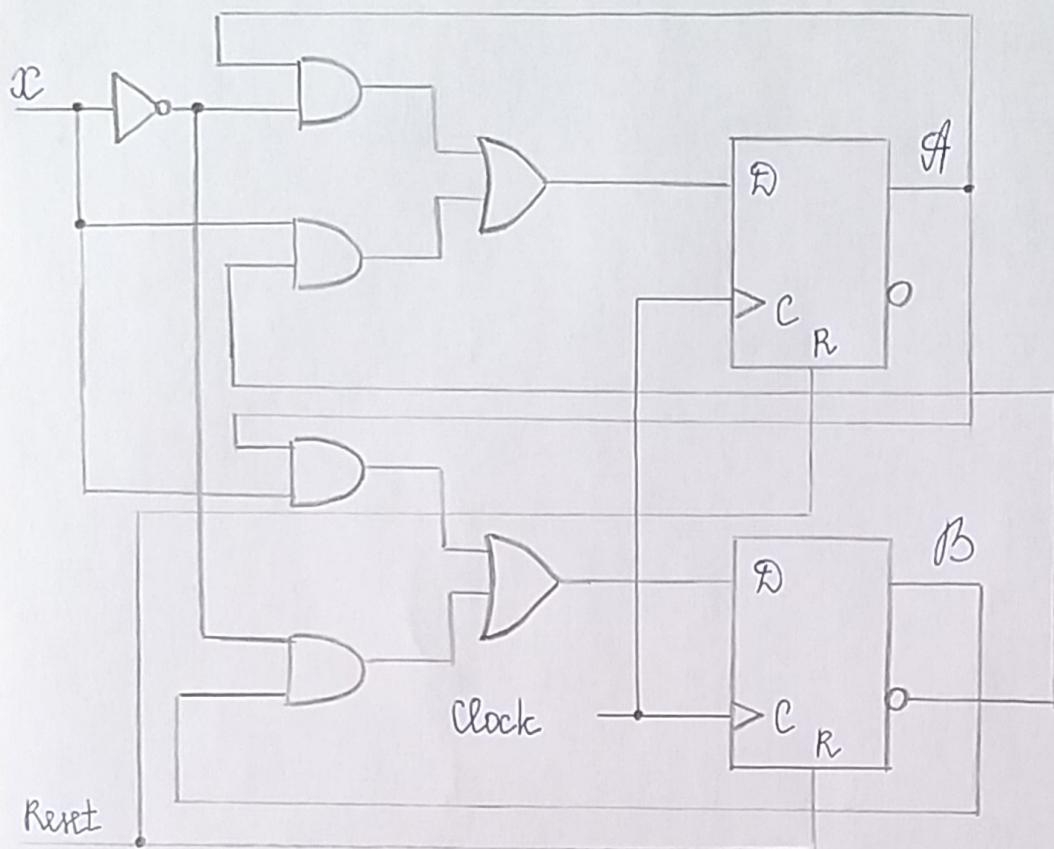

7. a) State table:

Current state	Input X	Next state	Output Z
A	0	B	0
A	1	D	0
B	0	D	0
B	1	C	0
C	0	A	0
C	1	F	0
D	0	F	1
D	1	C	1
E	0	C	1
E	1	E	1
F	0	E	1
F	1	F	1


B) State assignment:

Gray Code Assignment is used, and the least significant bit is equal to output:


$$A=000, B=010, C=110, D=001, E=011, F=111$$

100, 101 - don't care conditions



Current state			Next state		Output
A	B	C	$X=0$	$X=1$	Z
0	0	0	010	001	0
0	0	1	111	110	1
0	1	1	110	011	1
0	1	0	001	110	0
1	1	0	000	111	0
1	1	1	011	111	1
1	0	1	XXX	XXX	X
1	0	0	XXX	XXX	X

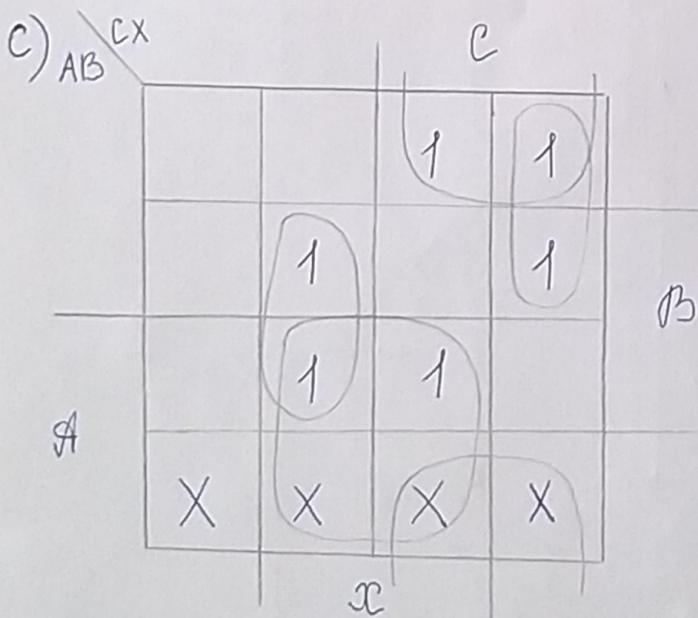
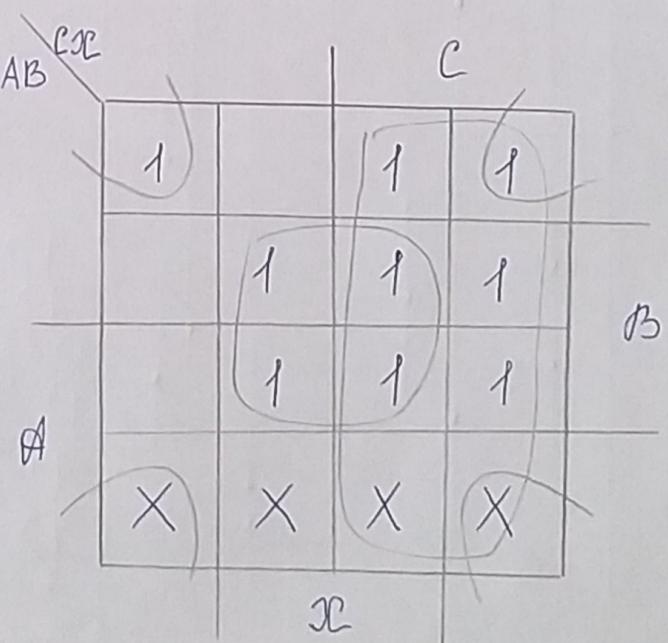
$$D_A = \alpha C + \bar{\alpha} \bar{C} + \beta \bar{C} C + \bar{\beta} C \bar{C}$$



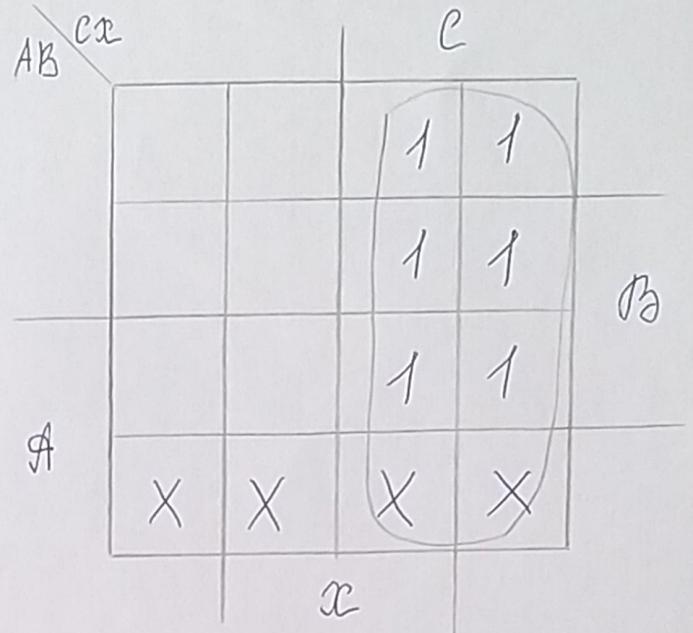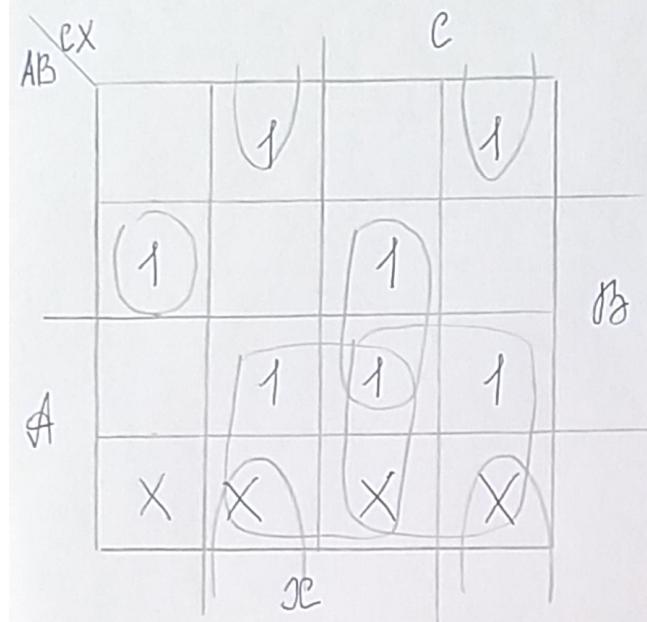
$$\mathcal{D}_B = C + B\mathcal{R} + \bar{B}\bar{\mathcal{R}}$$




$$D_C = AB + AC + BCX + \bar{B}C\bar{A} + \bar{B}\bar{C}X + \bar{A}\bar{B}\bar{C}\bar{X}$$


$$Z = C$$

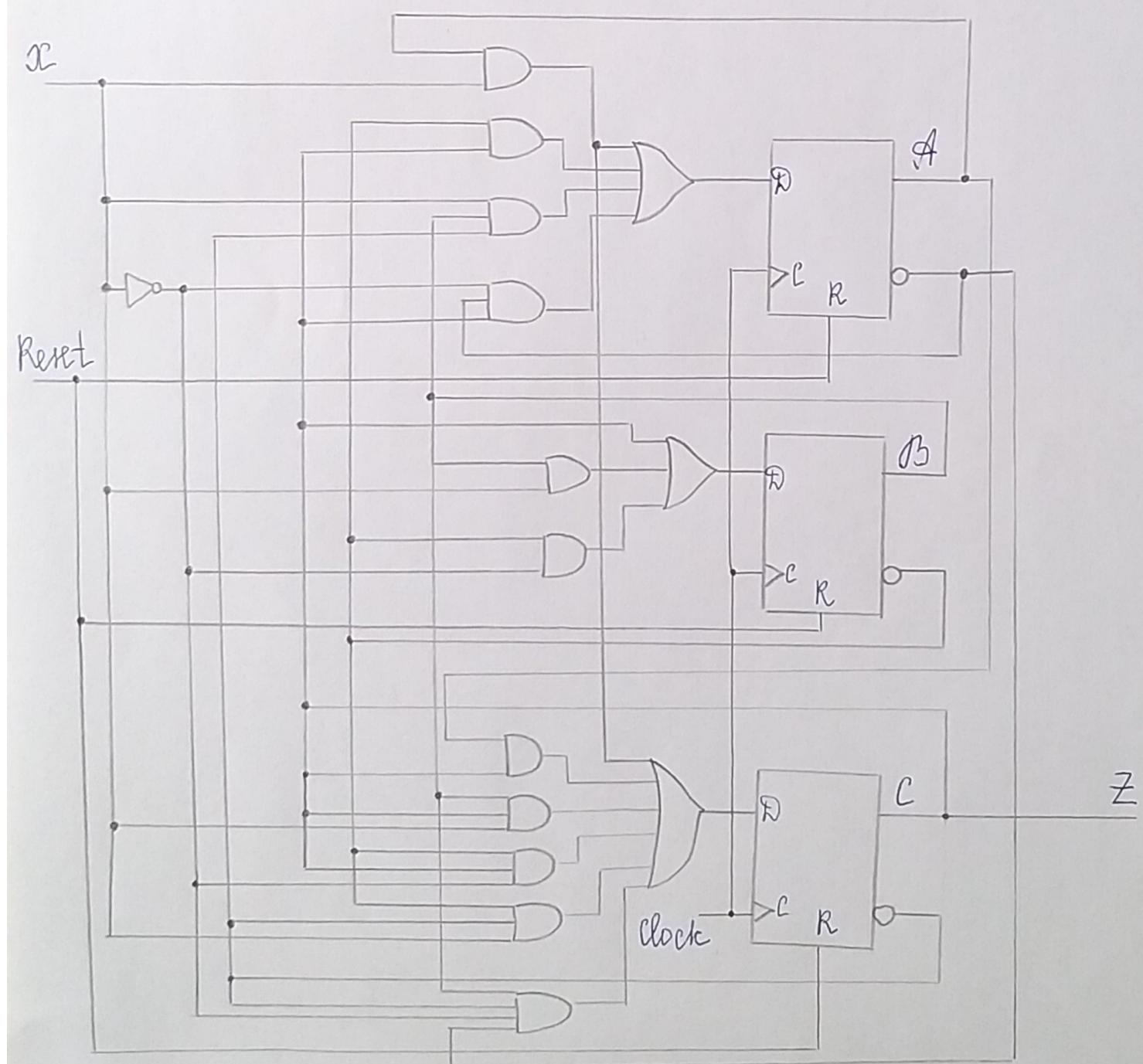

Technology mapping

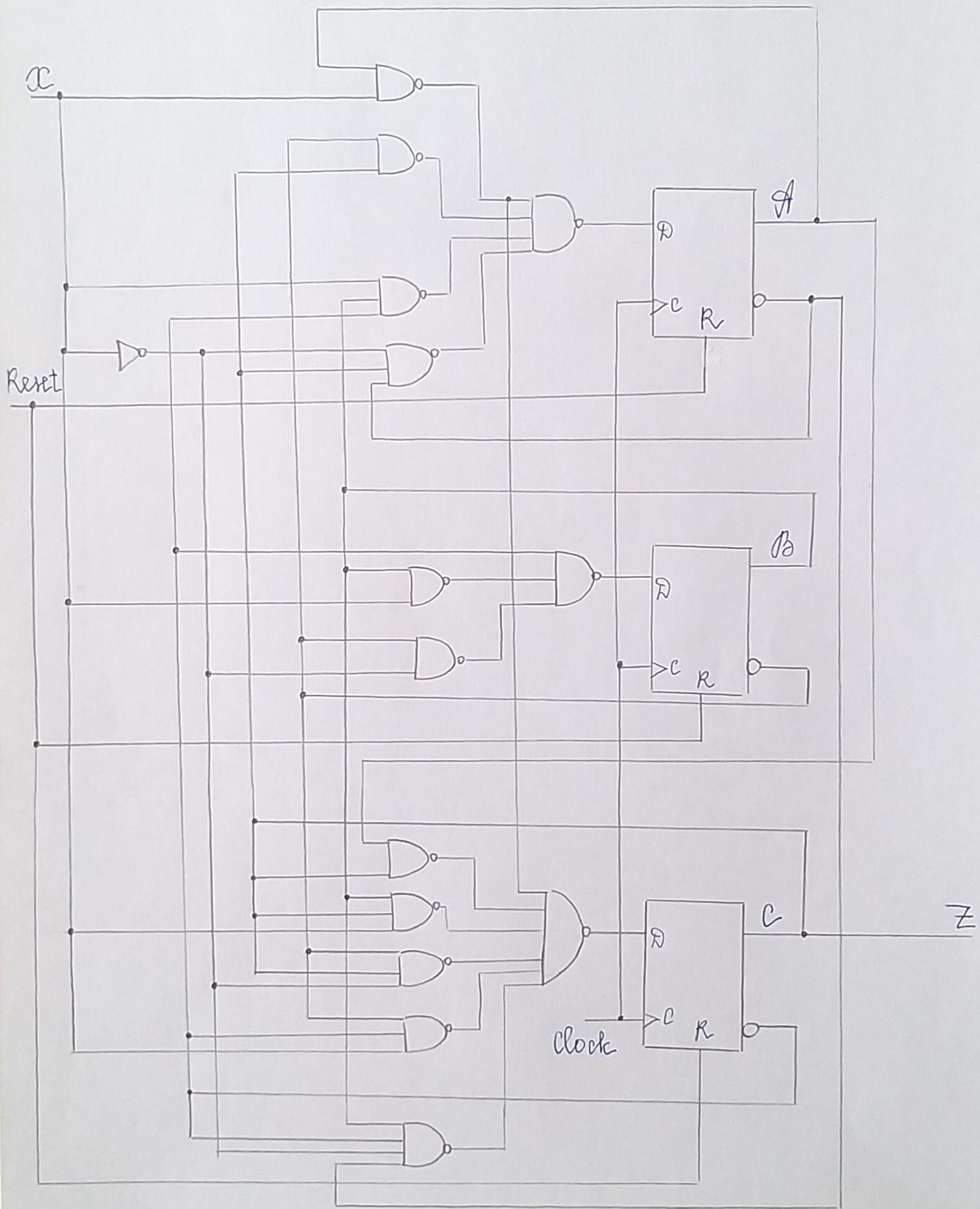

8. a) State diagram:

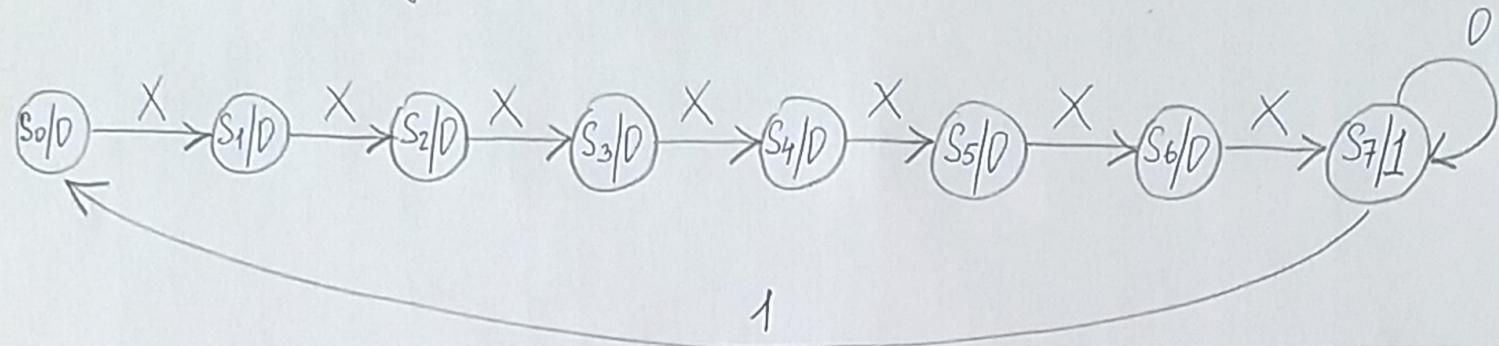


b) State table:


Current state	Next state $E=0$	Next state $E=1$	Output Z
S_0	S_1	S_1	0
S_1	S_2	S_2	0
S_2	S_3	S_3	0
S_3	S_4	S_4	0
S_4	S_5	S_5	0
S_5	S_6	S_6	0
S_6	S_7	S_7	0
S_7	S_7	S_0	1

State assignment:


Current state			Next state $E=0$	Next state $E=1$	Output Z
A	B	C			
0	0	0	001	001	0
0	0	1	010	010	0
0	1	0	011	011	0
0	1	1	100	100	0
1	0	0	101	101	0
1	0	1	110	110	0
1	1	0	111	111	0
1	1	1	111	000	1

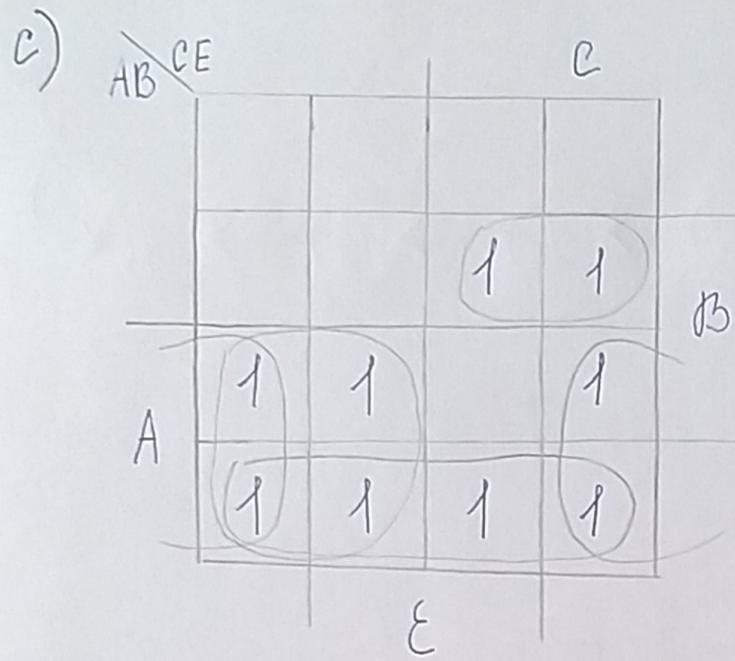

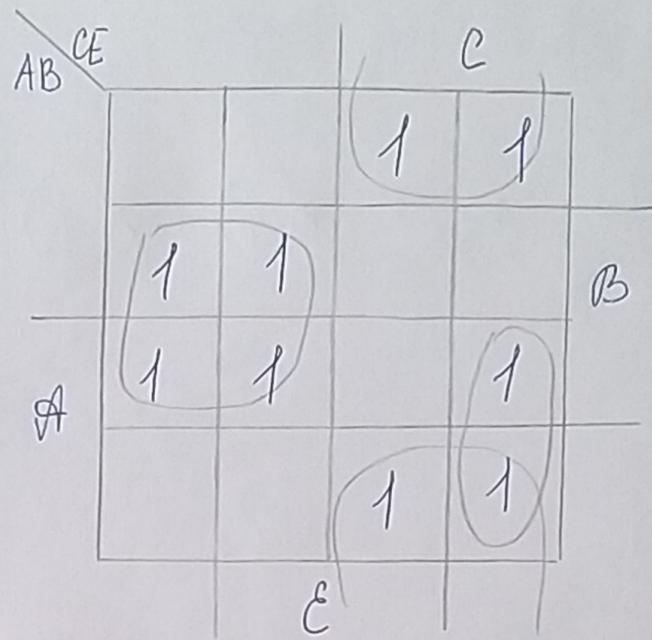
$$\mathcal{D}_A = \bar{A}\bar{C} + A\bar{B} + A\bar{E} + \bar{A}BC$$


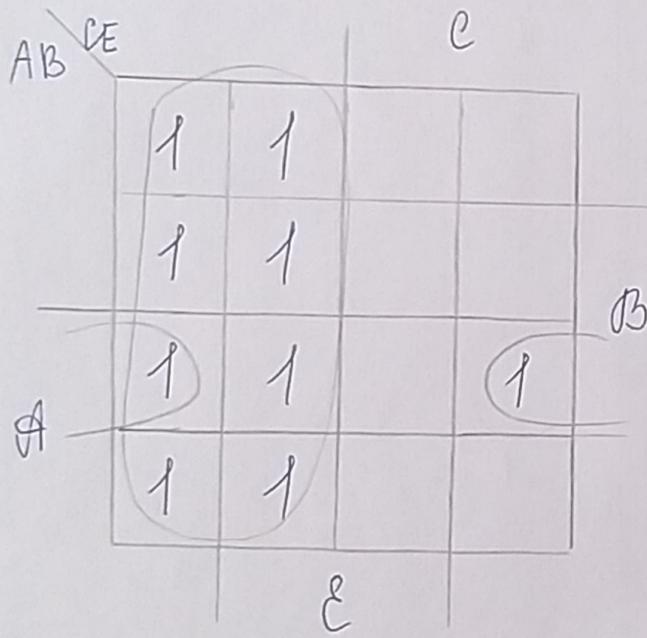
$$\mathcal{D}_B = B\bar{C} + \bar{B}C + AC\bar{E}$$



$$\mathcal{D}_C = \bar{C} + AB\bar{E}$$

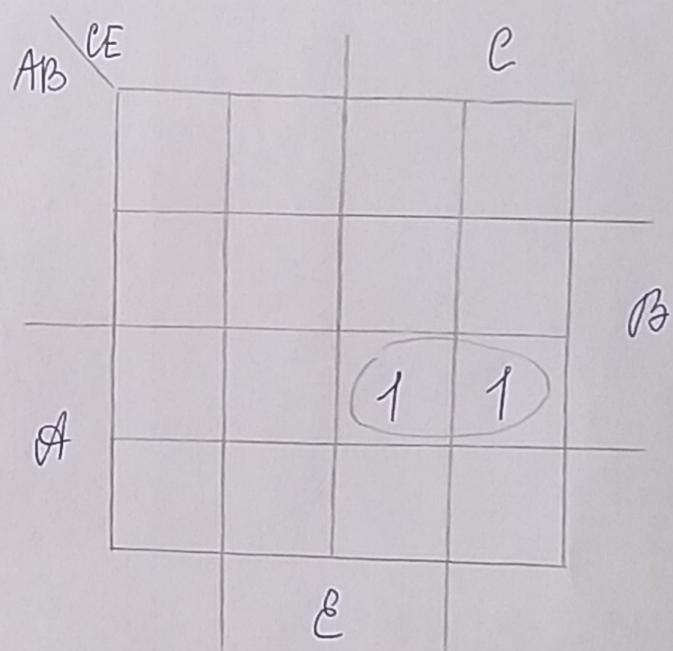

$$Z = ABC$$

Flip-flop input equations:

$$\mathcal{D}_A = A(\bar{C} + \bar{B} + \bar{E}) + \bar{A}BC$$

$$\mathcal{D}_B = B \oplus C + AC\bar{E}$$

$$\mathcal{D}_C = \bar{C} + AB\bar{E}$$

Output equation:

$$Z = ABC$$

Logic diagram:

